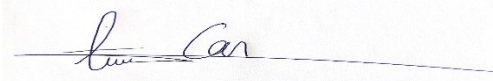




İZMİR
KÂTİP ÇELEBİ
UNIVERSITY

2010

Midterm Project	
Course Name:	EEE306-Power Systems
Date:	22.05.2020
Name and Surname:	Turhan Can Kargin
Student Number:	150403005
Signature	

ABSTRACT


In this assignment, power flow solution of the system was performed both with hand calculation and with MATLAB m-file code by using Gauss-Seidel method. Initial estimates of $V_2(0) = 1 + j0$ pu and $V_3(0) = 1.03 + j0$ and keeping $|V_3| = 1.03$ pu, and the phasor values of V_2 and V_3 was determined by performing three iterations.

Problem Solution:

Last two digit of my student number is 05 so, Voltage magnitude at bus 3 is fixed at 1.03 pu with a real and reactive power generation of 205 MW, 90.5 MVar, respectively.

100 MVA Base Value ;
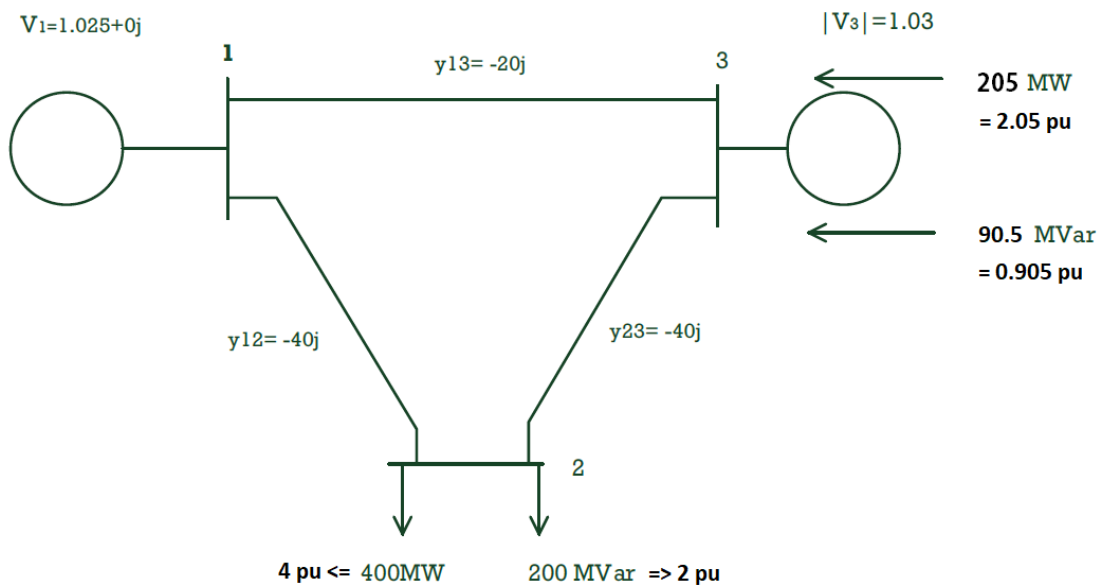
$$\frac{400\text{MW}}{100} = 4 \text{ pu}, \frac{200\text{MVar}}{100} = 2 \text{ pu}, \frac{205\text{MW}}{100} = 2.05 \text{ pu}, \frac{90.5\text{MVar}}{100} = 0.905 \text{ pu}$$



- Admittance of each line,

$$Y_{12} = Y_{21} = Y_{32} = Y_{23} = -j40$$

$$Y_{13} = Y_{31} = -j20$$

- The admittance matrix is given as,

$$Y_{bus} = \begin{bmatrix} Y_{12+13} & -Y_{12} & -Y_{13} \\ -Y_{21} & Y_{21+23} & -Y_{23} \\ -Y_{31} & -Y_{32} & Y_{31+32} \end{bmatrix}$$

$$Y_{bus} = \begin{bmatrix} -j60 & j40 & j20 \\ j40 & -j80 & j40 \\ j20 & j40 & -j60 \end{bmatrix}$$

- Gaus Seidal Power Flow Method

The power for **generator** bus are taken as **positive** while the power for **load** buses are taken as **negative**. For given system;

$$V_1 = 1.025 + j0, V_2^{(0)} = 1 + j0, V_3^{(0)} = 1.03 + j0$$

1) First Iteration

$$V_2^{(1)} = \frac{1}{Y_{22}} \left[\frac{P_2 - jQ_2}{V_2^{(0)*}} - Y_{21} \cdot V_1^{(0)} - Y_{23} \cdot V_3^{(0)} \right]$$

$$V_2^{(1)} = \frac{1}{-j80} \left[\frac{-4 + j2}{1} - j40 \times 1.025 - j40 \times 1.03 \right]$$

$$V_2^{(1)} = 1.003746 \angle -2.8553 \text{ pu}$$

$$V_3^{(1)} = \frac{1}{Y_{33}} \left[\frac{P_3 - jQ_3}{V_3^{(0)*}} - Y_{31} \cdot V_1^{(0)} - Y_{32} \cdot V_2^{(1)} \right]$$

$$V_3^{(1)} = \frac{1}{-j60} \left[\frac{2.05 - j0.905}{1.03} - j20 \times 1.025 - j40 \times 1.003746 \angle -2.8553 \right]$$

$$V_3^{(1)} = 1.02464 \angle -0.009062 \text{ pu}$$

2) Second Iteration

$$V_2^{(2)} = \frac{1}{Y_{22}} \left[\frac{P_2 - jQ_2}{V_2^{(1)*}} - Y_{21} \cdot V_1^{(0)} - Y_{23} \cdot V_3^{(1)} \right]$$

$$V_2^{(2)} = \frac{1}{-j80} \left[\frac{-4 + j2}{1.003746 \angle 2.8553} - j40 \times 1.025 - j40 \times 1.02464 \angle -0.009062 \right]$$

$$V_2^{(2)} = 0.9986 \angle -2.7797 \text{ pu}$$

$$V_3^{(2)} = \frac{1}{Y_{33}} \left[\frac{P_3 - jQ_3}{V_3^{(1)*}} - Y_{31} \cdot V_1^{(0)} - Y_{32} \cdot V_2^{(2)} \right]$$

$$V_3^{(2)} = \frac{1}{-j60} \left[\frac{2.05 - j0.905}{1.02464 \angle 0.009062} - j20 \times 1.025 - j40 \times 0.9986 \angle -2.7797 \right]$$

$$V_3^{(2)} = 1.02134 \angle 0.05932 \text{ pu}$$

3) Third Iteration

$$V_2^{(3)} = \frac{1}{Y_{22}} \left[\frac{P_2 - jQ_2}{V_2^{(2)*}} - Y_{21} \cdot V_1^{(0)} - Y_{23} \cdot V_3^{(2)} \right]$$

$$V_2^{(3)} = \frac{1}{-j80} \left[\frac{-4 + j2}{0.9986 \angle -2.7797} - j40 \times 1.025 - j40 \times 1.02134 \angle 0.05932 \right]$$

$$V_2^{(3)} = 0.9969 \angle -2.7752 \text{ pu}$$

$$V_3^{(3)} = \frac{1}{Y_{33}} \left[\frac{P_3 - jQ_3}{V_3^{(2)*}} - Y_{31} \cdot V_1^{(0)} - Y_{32} \cdot V_2^{(3)} \right]$$

$$V_3^{(3)} = \frac{1}{-j60} \left[\frac{2.05 - j0.905}{1.02134 \angle -0.05932} - j20 \times 1.025 - j40 \times 0.9969 \angle -2.7752 \right]$$

$$V_3^{(3)} = 1.02022 \angle 0.07244 \text{ pu}$$

Iteration Number	V1	V2	V3
0	1.025 \angle 0 pu	1.00 \angle 0 pu	1.03 \angle 0 pu
1	1.025 \angle 0 pu	1.003746 \angle - 2.8553 pu	1.02464 \angle - 0.009062 pu
2	1.025 \angle 0 pu	0.9986 \angle - 2.7797 pu	1.02134 \angle 0.05932 pu
3	1.025 \angle 0 pu	0.9969 \angle - 2.7752 pu	1.02022 \angle 0.07244 pu

Problem MATLAB Solution:

```
% Turhan Can Kargin - 150403005
% EEE306-Power Systems
% Midterm Project
% Due: 22.05.2020
% Power flow/ Load flow solution by the gauss seidel method
clear all;
clc;
%Formation of Admittance matrix
%line data matrix formation
%Line data |From bus| To Bus |Transfer admittance|
Ldata = [ 1      2      -40.0i
          1      3      -20.0i
          2      3      -40.0i];
Lo=Ldata(:,1);
Lt=Ldata(:,2);
yL=Ldata(:,3);
```

```

bus_no=max(max(Lo),max(Lt));
branch_no=length(Lo);
%Zero matrix formation
YB=zeros(bus_no,bus_no);
%For off diagonal elements
for k=1:branch_no
    YB(Lo(k),Lt(k))=-yL(k);
    YB(Lt(k),Lo(k))=YB(Lo(k),Lt(k));
end
%For diagonal elements
for m=1:bus_no;
    for n=1:branch_no
        if Lo(n)==m
            YB(m,m)=YB(m,m)+yL(n);
        else
            if Lt(n)==m
                YB(m,m)=YB(m,m)+yL(n);
            end
        end
    end
end
end
% Bus type and bus data matrix formation
%-----%
%| bus | Pgi | Qgi | Pli | Qli | ViR+ViI*j|
%| no  |     |     |     |     |          |
Busdata=[ 1      0.00  0.00  0.00  0.00  1.025+0.00i;
          2      0.00  0.00  4.00  2.00  1.00+0.00i;
          3      2.05  0.905  0.00  0.00  1.03+0.00i;];
GenMw=Busdata(:,2);
GenMvar=Busdata(:,3);
LoadMw=Busdata(:,4);
LoadMvar=Busdata(:,5);
V=Busdata(:,6);
Pb=GenMw-LoadMw;
Qb=GenMvar-LoadMvar;
itmax=3; % Question is asking for 3 iteration
%Formation of gauss seidal method
for it=1:itmax
    for i=2:bus_no
        SigVY=0;
        for j=1:bus_no
            if j~=i
                SigVY=SigVY+YB(i,j)*V(j);
            end
        end
        V(i)=(1/YB(i,i))*((Pb(i)-Qb(i))/((conj(V(i))))-SigVY)% Our Formula
    end
end
end
YB
V

%Command Window

YB =


    0.0000 -60.0000i    0.0000 +40.0000i    0.0000 +20.0000i
    0.0000 +40.0000i    0.0000 -80.0000i    0.0000 +40.0000i
    0.0000 +20.0000i    0.0000 +40.0000i    0.0000 -60.0000i

V =

    1.0250 + 0.0000i
    1.0245 - 0.0229i
    1.0246 + 0.0034i

```

Conclusion:

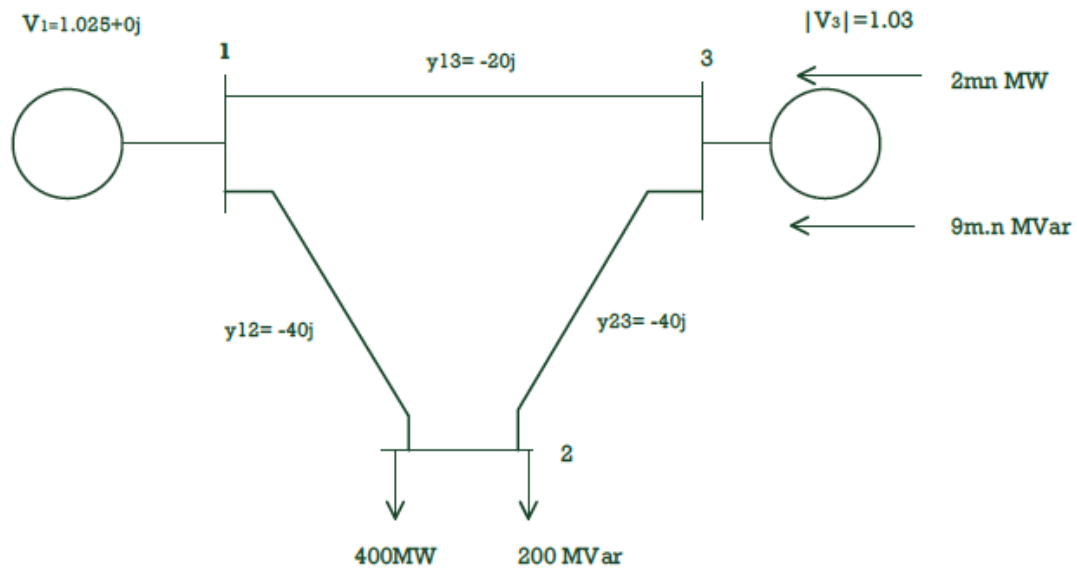

$$\underline{m = 0 \quad n = 5}$$

In this study, our aim is to determine phasor values of V_2 and V_3 by using Gauss-Seidel method with three iterations which the system is the above given figure one-line diagram of a simple three-bus power system with generation at buses 1 and 3. The voltage at bus 1 is $V_1 = 1.025 \angle 0^\circ$ per unit. Voltage magnitude at bus 3 is fixed at 1.03 pu with a real and reactive power generation of 2mn MW, 9m.n MVar, respectively. A load consisting of 400 MW and 200 MVar is taken from bus 2. Line admittances are marked in per unit on a 100 MVA base. Firstly, the hand calculation was performed and then MATLAB m-file solution is performed. Finally, it was determined that according to result hand calculation and MATLAB solution results are very similar.